



Mattrix Attenuator Applications

Single Ended

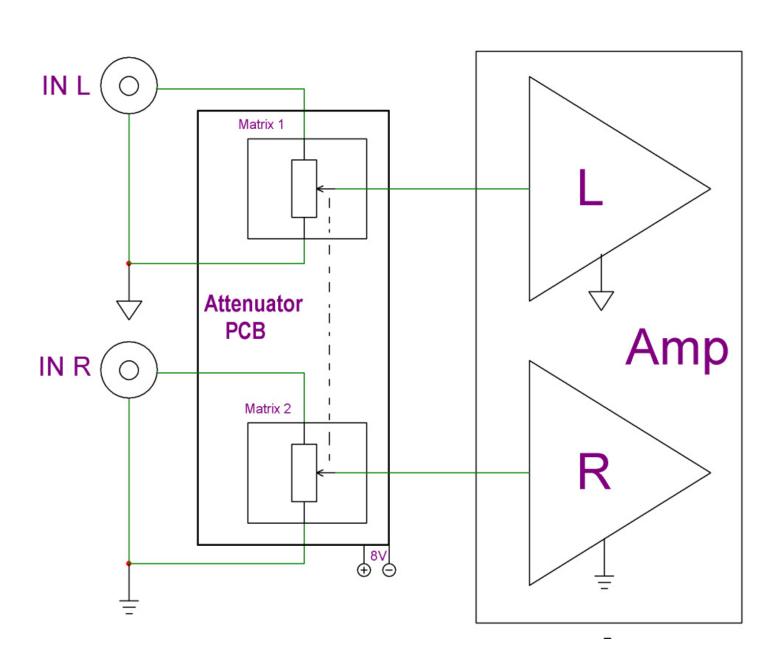

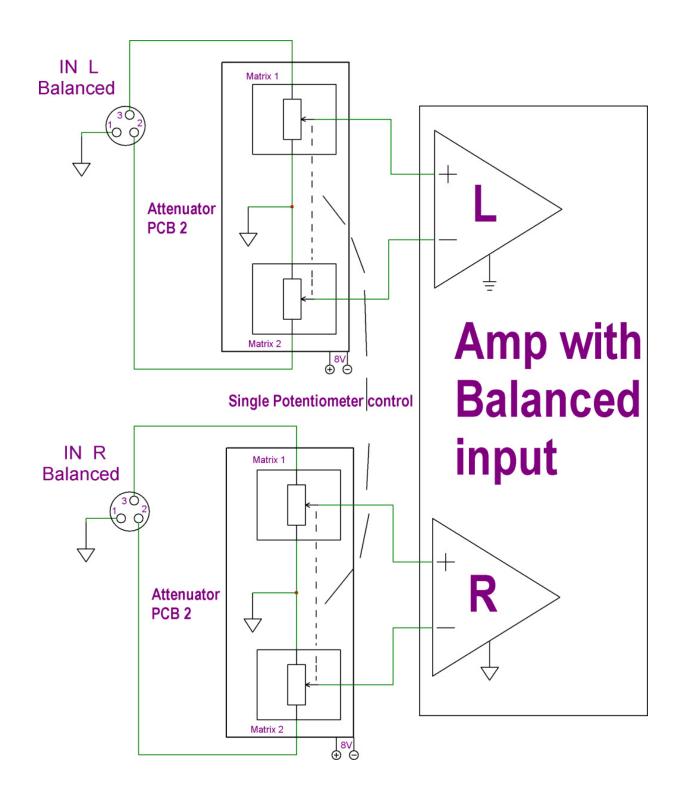


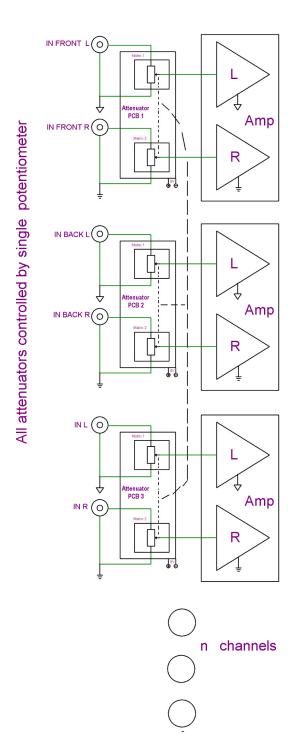


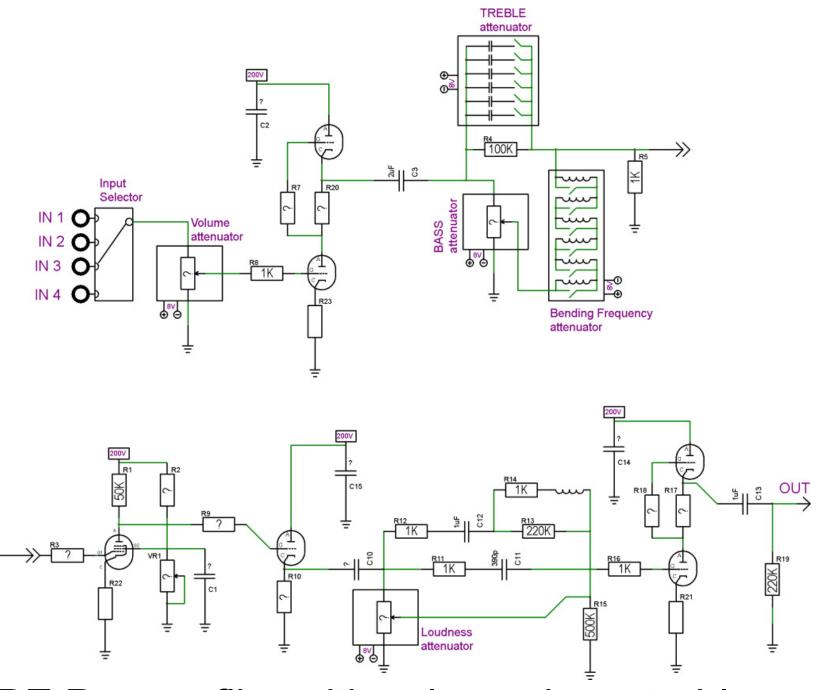


TUBE Preampflier with volume, bass, treble and loudness control

Input Impedance Selector

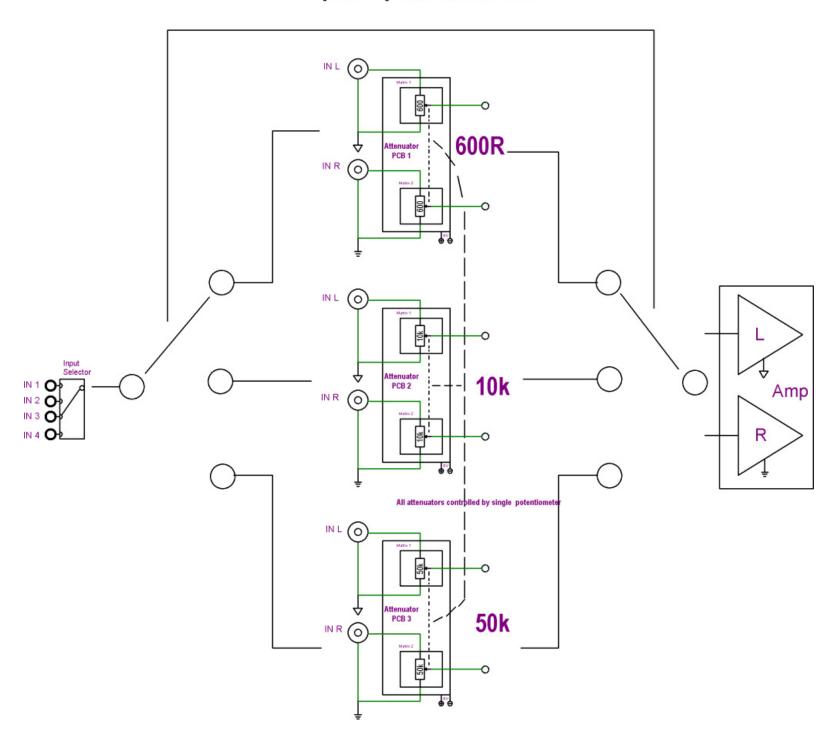


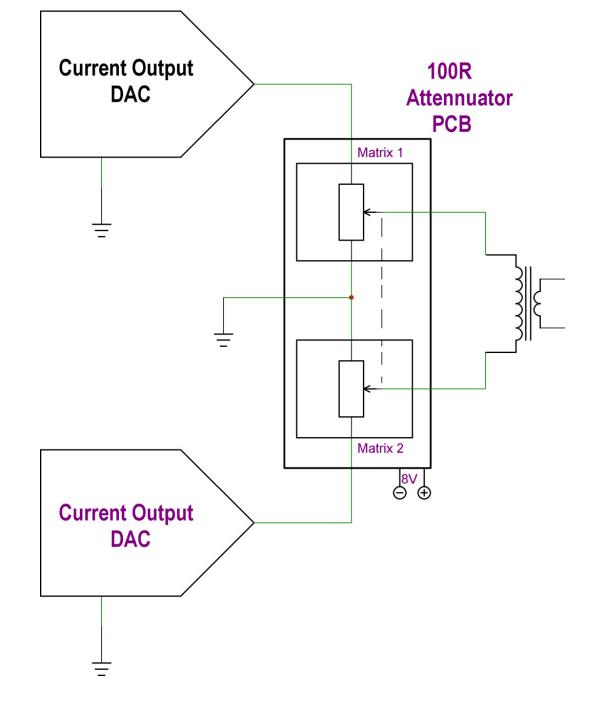

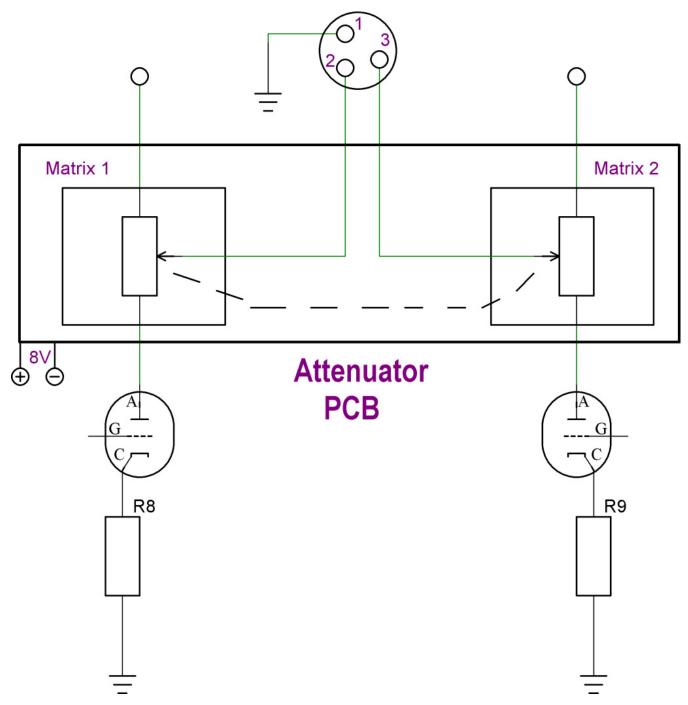
Balanced load and attenuation for current output DAC



Balanced Attenuated output

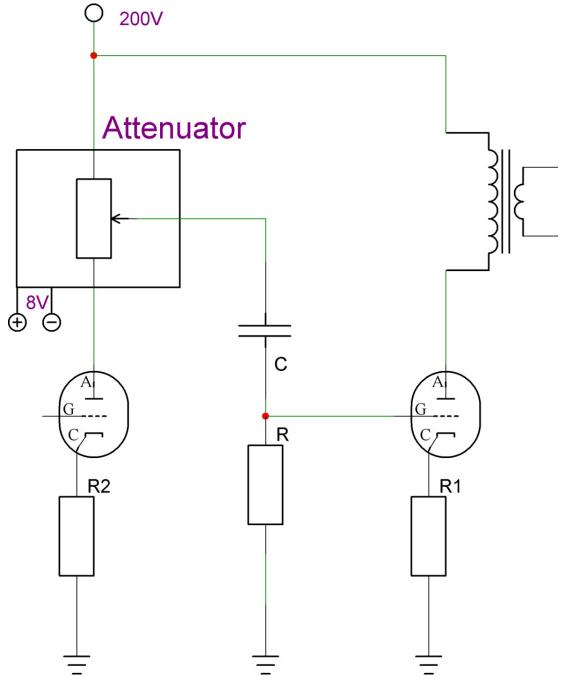

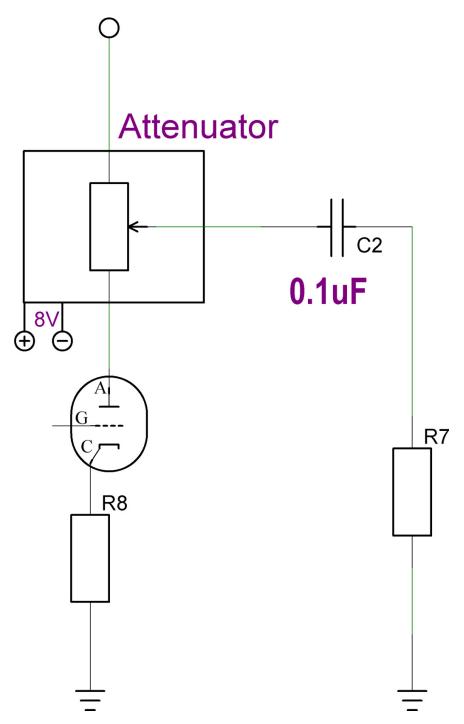Variation of Anode resistor eliminates input attenuation element



Variation of preamplifier's amplification using anode resistor